


L330 ADJUSTABLE POWER SWITCH




1x potentiometer



1x A/B switch

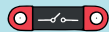

1x switch

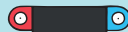

1x battery



4x



3x



1x



1x resistor 1k Ω



1x resistor 100 Ω



1x LED

By combining a switch and a potentiometer, you can build a circuit where the switch can be used to select a constant brightness, or continuous LED brightness control with a potentiometer.

