


L450 BRIGHTNESS CONTROL



1x LED




1x potentiometer

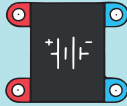

1x battery



1x

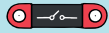

1x switch



1x resistor 100Ω

With the potentiometer you can directly control the current flowing through the LED diode and thus change its brightness. A small resistor in series serves as a current limiter when the potentiometer is set to the extreme position where it has zero resistance.

