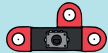


L440 COMMON EMITTER AMPLIFIER WITH NPN AND BULB



1x potentiometer



1x transistor NPN



1x bulb




1x switch



1x resistor 10kΩ



1x

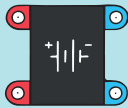

1x battery



1x



3x



2x

By changing the low current to the transistor base, you can control the high current flowing through the bulb since opening and closing the transistor causes the voltage on the bulb to change. We use an NPN transistor in this case.

