

L420 PNP AMPLIFIER WITH COMMON COLLECTOR I.



1x potentiometer



1x transistor PNP




1x bulb



1x switch



1x resistor 1kΩ

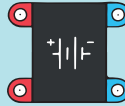

1x battery



2x



2x

Functionally, it is the same circuit as the emitter follower with NPN, just with a transistor of opposite conductivity. The base current flows in the opposite direction; therefore, it is necessary to modify the base circuit accordingly.

