 



L20 LED WITH SWITCH



1x LED



1x resistor 1kΩ

 

1x battery



1x



1x switch



3x

A basic build with an LED as a light source. LEDs are not adjusted to the supply voltage of a battery, therefore it is necessary to add a series resistor to the build. That will lower the current flow in the circuit. Otherwise the LED would be destroyed.

