

S60 MORSE CODE




1x speaker



1x transistor PNP



1x transistor NPN

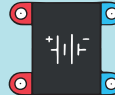

1x battery



2x



1x



1x button



1x capacitor 100nF



1x resistor 100kΩ



1x

A simple buzzer with a button to practice the Morse code. This is a modified S40 circuit, where the selection of components achieves the characteristic tone used to receive Morse codes.

