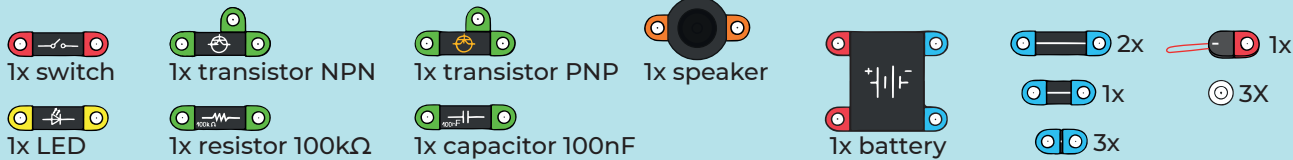


S20 MULTIPLE-TONE GENERATOR II.



We replace the buzzer with a capacitor with a capacitance of 100 nF. The capacitance is higher, and the tone pitch decreases. Again, the LED only appears to be constantly lit, but the brightness has changed. A good eye can already notice a hint of flicker – like rapid fluctuations in brightness.

