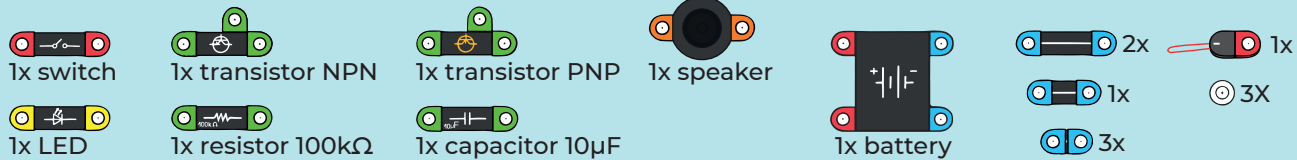


### S30 MULTIPLE-TONE GENERATOR III.



Replace the capacitor with a capacitance of 100 nF with a capacitor with a capacitance of 10 μF. This capacitance is many times higher, and the continuous tone falls apart into mere clicking. The LED flashes. The generator frequency has dropped below the limit that a person can audibly perceive as a continuous tone.

