


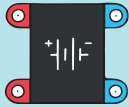





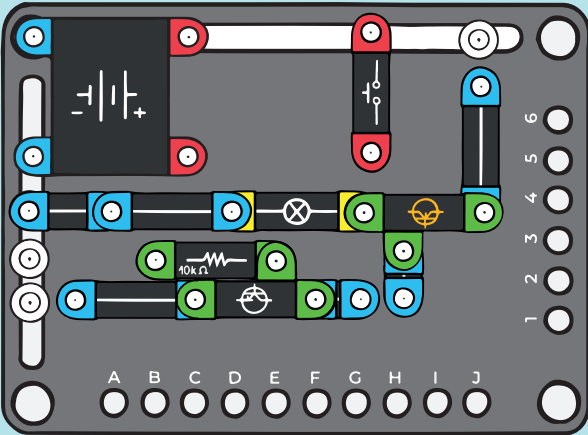


# L580 NIGHT LIGHT AUTOMATIC SWITCH-OFF V.

-   
 1x bulb
-   
 1x transistor PNP
-   
 1x transistor NPN
-   
 1x battery
-   
 3x
-   
 3x
-   
 1x
-   
 1x
-   
 5x

A simplified version without the Schmitt circuit. The circuit works similarly to L570 however, in the absence of a Schmitt circuit, it causes an undesirably slow dimming of the light.

1.



2.

