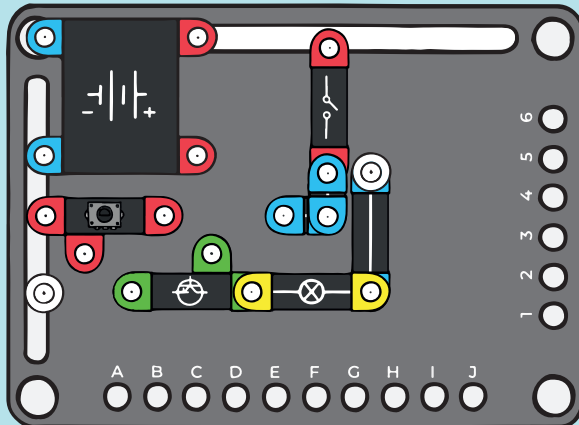


L300 NPN AMPLIFIER WITH LED IN REVERSE DIRECTION



This build uses the same circuit as the previous one, just with the LED connected in the reverse direction. Therefore, no current flows into the transistor base and the bulb does not give light.

1.



2.

