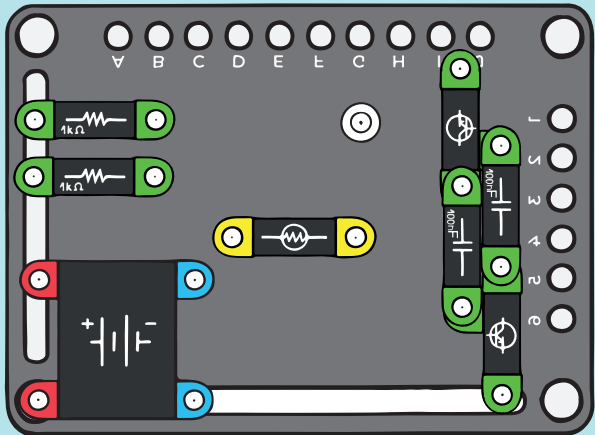


S100 PHOTSENSITIVE ELECTRONIC ORGAN

- 1x fotoresistor
- 2x transistor NPN
- 2x resistor 1kΩ
- 2x capacitor 100nF
- 1x buzzer
- 2x resistor 10kΩ
- 1x battery
- 1x potentiometer
- 2x jumper (red/black)
- 2x jumper (blue/black)

You can connect a photoresistor instead of a potentiometer so the pitch will be directly proportional to the degree of illumination of the photoresistor.

1.



2.

