


L180 POLARITY INDICATOR



2x LED



1x resistor 1kΩ

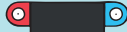

1x battery



3x



1x switch



1x battery



1x

Two anti-parallel LEDs indicate the polarity of the power supply. The LEDs light up alternately depending on the battery orientation. Try connecting the battery the other way – you will see that the second LED lights up.

