

## L430 PNP AMPLIFIER WITH COMMON COLLECTOR II.



1x potentiometer



1x transistor PNP




1x bulb



1x switch



1x resistor 100 $\Omega$

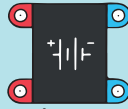

1x battery



2x



2x

Changing the base resistor to a low value of 100  $\Omega$  will increase the current flowing to the transistor base, but the bulb brightness remains almost constant. This is because the voltage on the bulb still corresponds to that on the potentiometer slider although the circuit would be able to supply more current. However, since the load is still just one bulb, the amount of current consumed does not increase, so changing the resistor has virtually no effect.

