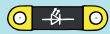



## L340 SAFETY BUTTON



1x LED



1x resistor 1k $\Omega$

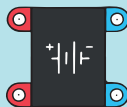

1x battery



1x



2x button

Two buttons connected in series close the circuit only if both buttons are pressed. The circuit closure is indicated by the LED. In practice, this connection is used as a safety element for dangerous machines (e.g. when material needs to be loaded manually under a press) where the operator must press two buttons with both hands to activate the machine. This ensures that both hands are out of the dangerous parts of the machine, which prevents injuries.

