

L130 SWITCHING LEDs




2x LED



1x resistor 1kΩ



1x A/B switch

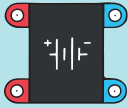

1x battery



1x




1x



2x

The changeover switch is a variant of the on-off switch that has both positions of the switching contact available. When the changeover switch is operated, the contact interrupts the current flow in one part of the circuit and, at the same time, closes another part of the circuit. The LED therefore lights up alternately, depending on the position of the changeover switch. However, only one LED is active at any point of time.

1.

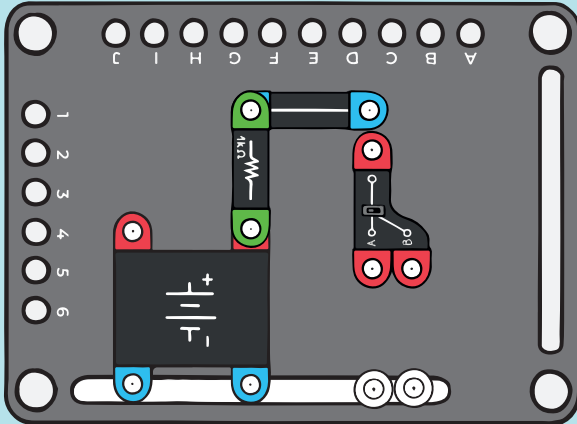

2.

