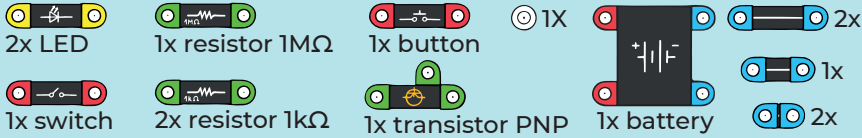


L320 SWITCHING WITH BUTTON II.



To switch between the red and the white LEDs, we used significantly different properties of both LEDs (different lighting voltages). However, if you want to switch similar or the same LEDs, you need to choose a different solution. You can use a PNP transistor. In this case, it acts as a switch that opens (and thus the corresponding LED goes out) if you press the button. At the same time, the button switches the second LED on, and it should light up when the button is pressed.

