

## E40 YOUR OWN BATTERY II.




1x A/B switch



1x switch




1x resistor 1kΩ

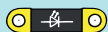

1x LED



2x capacitor 100µF

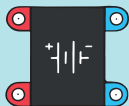

1x battery



1x



2x

This build is identical to the previous version but contains two capacitors connected in parallel. The capacitor bank thus has a double capacitance. The LED will light up for a longer time.

